

Technical Data of Crystal Unit								
MURATA Part No.: XRCMD48M000FXQ60R0								
Applied to R5F11FLL								
Compatibility Information								
IC is compatible to : R5F11FLJ R5F11FLK								
Murata Manufacturing Co., Ltd.								



## ■ Murata's recommendation 推奨回路定数

İtem			Condition	
IC name		IC名		R5F11FLL
Parts Number of Crystal Unit		品番		XRCMD48M000FXQ60R0
Circuit Parameter	External	負荷容量	CL1	8pF
	load capacitance	負荷容量	CL2	9pF
	Feedback resistance	帰還抵抗	Rf	No mount
	Damping resistance	制限抵抗	Rď	0ohm
		制限抵抗	Rd	0ohm
Supply Voltage Range		電源電圧範	井	1.8 to 3.6V
Temp. Range		温度範囲		-30 to 85deg.C

Test Circuit

Set: 1.8 to 3.6V [?] Evaluation board R5F11FLL Rd' Rd≶ Crystal Unit 巾 VOUT VIN CL1 CL2

7/1

7/1

7/1

Measurement equipment

DSO6052(K) Oscilloscope Current probe CT-6(T) P5100A(T) Passive probe (40Mohm/2,5pF)

E3631A(K) DC supply Frequency counter 53181A(K) Sepectrum analyzer E4401B(K)

(K) Keysight (T) Tektronix

Crystal Unit : XRCMD48M000FXQ60R0 Set =1.8 to 3.6V CL1 =8pF

CL2 =9pF Rf : No mount Rd' =0ohm Rd =0ohm

Ta =-30 to 85deg.C

### ■ Characteristics of oscillation circuit on above condition 推奨定数での発振回路特性

7

7/1

Circuit Characteristics 特性	Value 測定値			Remarks 備考	
Center Frequency and Difference 発振回路における発振周波数とそのずれ量 (*1) (Typical sample at Set=3V,+25deg.C)	48.00	0003	[MHz]	Oscillating frequency and its shift against nominal frequency 発振回路における発振周波数と振動子の公称周波数に対す	
	0.	06	[ppm]	ずれ量	
Load Capacitance on your PCB 負荷容量値 (Typical sample at Set=3V,+25deg.C)	5.8 [p		[pF]	This value shows load capacitance the evaluated circuit has 発振回路において振動子の両端に仮想的に接続される容量	
Negative Resistance and Oscillation margin 負性抵抗/発振余裕度	-R	130	[Ω]	The details is explained in page 2 詳細につきましては、次頁をご参照下さい。	
(at Set=3V,+25deg.C)	Ratio	3.25	[Times]		
Drive Level ドライブレベル (Typical sample at Set=3V,+25deg.C)	30 [uW]		[uW]	Drive power of crystal under circuit condition 発振回路が動作している状態において振動子で消費される 電力	
Oscillating Voltage 発振電圧	VINp-p	0.8	[V]	Swing level at input side 発振入力振幅 (VIN_H - VIN_L)	
(Typical sample at Set=3V,+25deg.C)	VOUTp-p	0.8	[V]	Swing level at output side 発振出力振幅 (VOUT_H - VOUT_L)	
Oscillation Start up Time 起動時間 (*2) (Typical sample at Set=3V,+25deg.C)	0.38 [ms]		[ms]	Time to reach 90% of the oscillation level under steady state 定常状態の発振振幅の90%に達するまでの時間	

<sup>\*1</sup> Frequency difference means the oscillating frequency difference between your PCB and Murata's frequency sorting circuit. 貴社基板と当社検査回路では、同一振動子を使用した場合でも発振周波数の差が生じます。これを発振周波数相関と呼びます。 \*2 The measurement results is affected by the rise-up characteristics of supplied voltage on your PCB. 測定結果は実装基板の電源立ち上がり特性の影響を受けます。

The characteristics of the crystal oscillation circuit is affected by the circuit constants and actual mounting conditions and so on

Therefore, it is possible to get the different results from above one due to the production variation of the crystal oscillator circuitry.

In your company, please use this results after confirmation of the matching between our crystal unit and oscillator circuit.

And furthermore, since the above-mentioned evaluation results evaluate only an oscillating circuit block, please confirm the checking of operations of a set in your company.

注意事項 発振回路の特性は回路定数や実装状態により影響を受けるため、回路や基板のパラツキ等によっては上記の結果と異なる可能性があります。 貴社におかれましても弊社水晶振動子と発振回路とのマッチングをご確認の上、ご使用下さるようお願い致します。 また上記評価結果は発振回路ブロックのみを評価したものですので、セットの動作確認は貴社にてご確認下さるようお願い致します。

Murata Manufacturing Co., Ltd.



#### ■ Test Data : Characteristics of recommended conditions

# Center frequency Center frequency difference

48.000003 MHz

0.06 ppm from 48MHz

This frequency difference causes imbalance of initial frequency tolerance on your PCB, because of load capacitance difference.

## Load capacitance of the circuit

This value shows load capacitance the evaluated circuit has.

Our crystal proposed in this report is sorted with 5.8pF as load capacitance

# **Negative resistance**

Ratio of negative resistance |-R| to R1spec.

#### 3.25 times Ratio

Ratio = |-R| / R1spec.

R| 130 ohm Negative resistance |-R| = Rs\_max + Re

100 ohm

Maximum series resistance for Crystal Unit to keep oscillation

Re: 30.0 ohm

Effective resistance of Crystal Unit at actual oscillation frequency

R1spec. 40 ohm
Equivalent series resistance

#### **Drive level**

Drive power of crystal under circuit condition shown in page 1

#### **Drive level** 30 uW

Drive level =  $I^2 \times R1$ 

22.1 ohm

Murata Manufacturing Co., Ltd.



